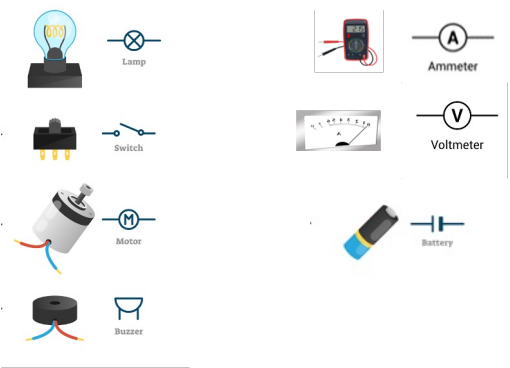





Lesson Sequence

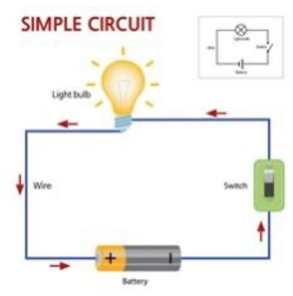-  1. Describe the parts of an electric circuit
-  2. Explore voltage and its effect on an electrical circuit
-  3. Apply knowledge to identify and correct problems in a circuit
-  4. Investigate what affects the output of a circuit
-  5. Build a set of traffic lights
-  6. Apply knowledge of conductors and insulators

Circuit Symbols





Wires are always drawn with a **straight line** using a **ruler** in scientific diagrams.





The **current** flows from negative to positive. There are no gaps so it is a **complete** circuit and the bulb lights up.

Different Circuits

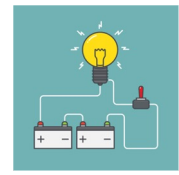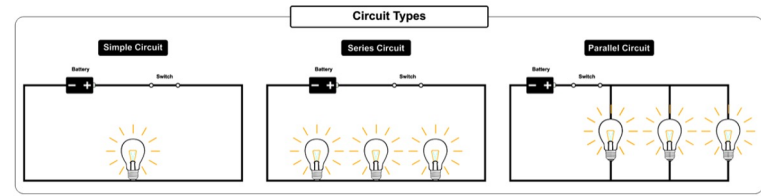

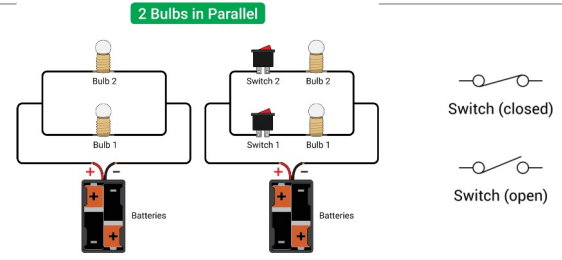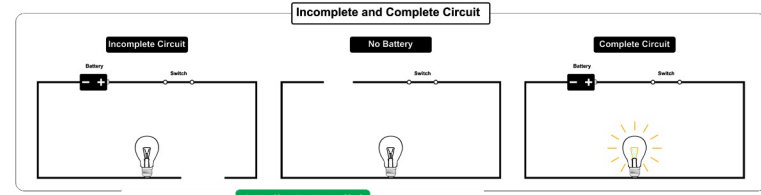Adding more cells (batteries) to a circuit will make bulbs **brighter**, buzzers **louder** and motors **faster**.




Switches can be placed in a **parallel circuit**, so that 1 light can be turned on while another is off (just like in a house).



Use the picture below to draw a scientific diagram of the circuit:



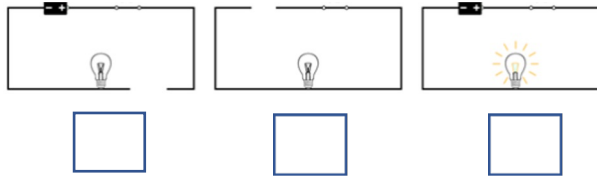Tick the circuits that work and cross the ones that don't.




Draw a line to match up the symbol with its correct name:

- closed switch
- buzzer
- lamp/bulb
- voltmeter
- open switch
- motor
- battery/cell
- ammeter

Explain 2 ways to make the bulbs in a circuit brighter:

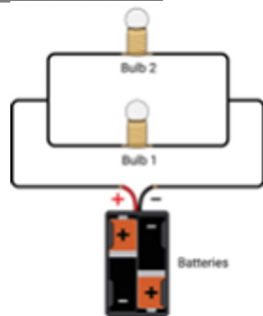1. _____
- _____
2. _____
- _____

Add 2 switches onto the diagram so that they turn on and off separately.














Unit Rocket Words: Electricity



Rocket Words

	component	The different pieces of equipment used to build a circuit.
	amps	A unit of measurement for electricity.
	voltage	A unit of measurement for electricity.
	voltmeter	A piece of equipment that measures the amount of electricity being used.
	ammeter	A piece of equipment that measures the amount of electricity being used.
	current	The flow of electricity around a circuit.
	output	The amount of energy produced in a circuit.
	complete circuit	A circuit where there are no gaps so an electrical current can flow.
	incomplete circuit	A circuit that has a switch open or gap caused by wires not connected, meaning the electrical current cannot flow.